

# Fundamentals of Computer Systems


## Finite State Machines

Timothy K Paine

Columbia University

Summer 2024


## Moore and Mealy Machines

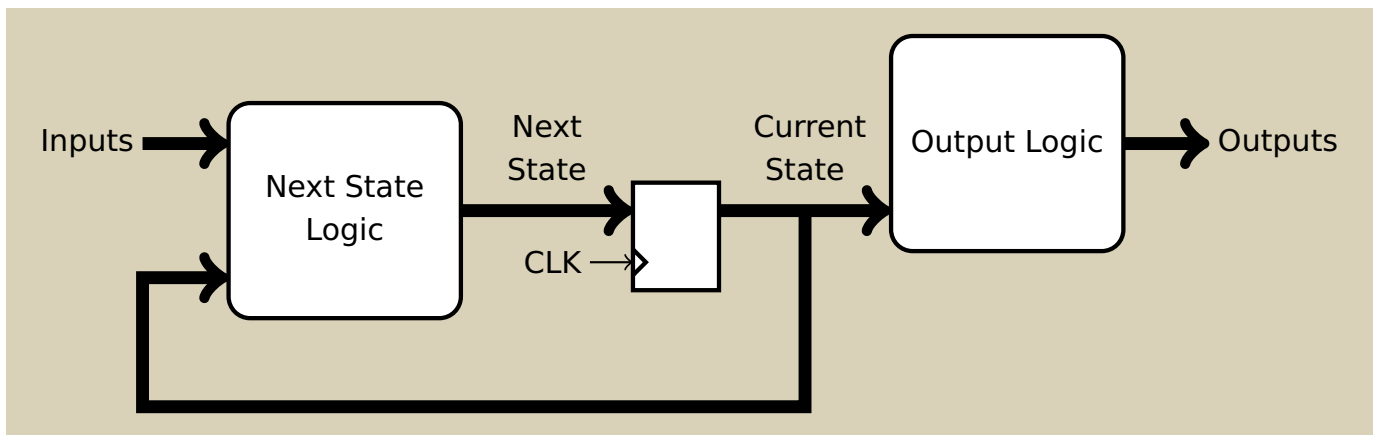

The Moore Form:

Outputs are a function of *only* the current state.

## Moore and Mealy Machines

 


The Mealy Form:

Outputs may be a function of *both* the current state and the inputs.

A mnemonic: *Moore* machines often have *more* states.

## Mealy Machines are the Most General

 


Another, equivalent way of drawing Mealy Machines


This is exactly the synchronous digital logic paradigm
 
## Moore vs. Mealy FSMs

Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last four digits it has crawled over are 1101. Design Moore and Mealy FSMs of the snail's brain.



 
## State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output
 
## State Transition Diagrams: Looking for “1101”



Moore Machine: States indicate output

 
## State Transition Diagrams: Looking for “1101”



Moore Machine: States indicate output



 
## State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output
 
## State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

 


Mealy Machine: Arcs indicate input/output
 
## State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

 


Mealy Machine: Arcs indicate input/output
 
## State Transition Diagrams: Looking for “1101”




Moore Machine: States indicate output

 


Mealy Machine: Arcs indicate input/output
 
## State Transition Diagrams: Looking for “1101”



Moore Machine: States indicate output

 


Mealy Machine: Arcs indicate input/output

## Moore Machine

Next State			Output	
Q	A	D	Q	Y
S0	0	S0	S0	0
S0	1	S1	S1	0
S1	0	S0	S2	0
S1	1	S2	S3	0
S2	0	S3	S4	1
S2	1	S2		
S3	0	S0		
S3	1	S4		
S4	0	S0		
S4	1	S2		

# Moore Machine

Next State			Output	
Q	A	D	Q	Y
000	0	000	000	0
000	1	001	001	0
001	0	000	010	0
001	1	010	011	0
010	0	011	100	1
010	1	010		
011	0	000		
011	1	100		
100	0	000		
100	1	010		

 


## Mealy Machine

<b>Q</b>	<b>A</b>	<b>D</b>	<b>Y</b>
S0	0	S0	0
S0	1	S1	0
S1	0	S0	0
S1	1	S2	0
S2	0	S3	0
S2	1	S2	0
S3	0	S0	0
S3	1	S1	1




# Mealy Machine


Q	A	D	Y
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	11	0
10	1	10	0
11	0	00	0
11	1	01	1

 
 
## More Intuitive (Non-Minimal) Solutions



Moore Form: Output Depends Only on State

 

Mealy Form: Output Depends on Input Immediately

# Finite State Machine Design Process

1. Create state transition diagram (abstract implementation of spec)
2. Select state encoding
3. Create tables for output and next state logic
4. Minimize output and next state logic
5. Wire up design (produce schematic)